



2B : Verilog for Synthesis

CG3207 Computer Architecture

Rajesh Panicker, ECE, NUS


General Rules for Synthesizability

- Do NOT use delays (`#delay`)

- Combinational (propagation) delays are hardware dependent*; not something the synthesis tool can insert based on HDL code


*controllable to some extent through timing constraints (.xdc file) such as `create_clock`, `set_max_delay`, `set_min_delay` etc.

 - Clock cycle delays are inserted by the designer explicitly by introducing a physical register (i.e., it is a part of your design), and not done automatically by the synthesis tool based on `#delay`




- Try to use only one clock for the entire design

 - Connect the input of every sequential element to this clock
 - Multiple clocks => more clocking resources, complicates timing analysis (related clocks), requires clock domain crossing circuitry (unrelated clocks)
- The clock should not come from a combinational circuit, as a combinational circuit can have glitches in its output



General Rules for Synthesizability...

 
- Do not use **posedge/negedge** for anything other than clock or reset of a sequential process. i.e., do not use something like **@(posedge button)** for detecting a transition
 - Use a synchronous edge detection scheme instead – i.e., by comparing the current value with the previous value stored in a register



```
assign button_edge = button & button_prev;


always @ (posedge CLK)
begin
    button_prev <= button;
end
```

 - Do not have combinational feedback paths
 - Every circular assignment should be broken by a register (an assignment in a synchronous **always** block)



```
assign Z = Y & A;

always @ (*)
begin
    A <= X | Z;
end
```

 


```
assign Z = Y & B;

always @ (posedge CLK)
begin
    B <= X | Z;
end
```


General Rules for Synthesizability...

 - **regs** and **wires** should not have multiple drivers
 - A **wire** should appear on the left-hand side of only one **assign** statement. A **reg** should appear on the LHS of only one **always** block



```
always @ (*)  
begin  
    Z <= A & B;  
end  
  
always @ (*)  
begin  
    Z <= X | Y;  
end
```

 - Ok to have a **reg** at the LHS of multiple statements within the same **always** block as long as the same type of assignment is used
 - Only blocking or only non-blocking, do not mix the two for a particular **reg**
 - The last assignment will determine the value of the **reg** after the **always** block execution




```
always @ (*)  
begin  
    Z = 1'b0;  
    if(~X) //else is implicit  
        Z = Y;  
end
```

General Rules for Synthesizability...

- Initializations of **regs** (through an **initial** block or by an assignment along with **reg** declaration, say **reg Z = 1'b0;**) are useful for initializing registers and memories for FPGAs, but are ignored by ASIC synthesis tools
 - **wires** cannot be meaningfully initialized as they don't store anything
 - Initialization to 0 or 1 will connect the wire to a constant 0 or 1 respectively. Further assignment using **assign** will lead to it having multiple drivers
 - **regs** that get synthesized as combinational* circuits cannot be meaningfully initialized
 - *Not all **regs** infer physical registers (we will see later)!
 - Do not assume registers and memory have 0s as initial value

 Circuitry (simplified) to initialize to 0.
Similar functionality is built into FPGAs and asserted when programming a bitstream (aka configuration);
need to be included explicitly for ASICs



- Every **always** should follow one of the three templates given in the following slides strictly. **Every single always**


I : Purely combinational



Combinational : all outputs[#] are SOP or POS functions of the current inputs [#]

- Every input must be present in the sensitivity list, or simply use **(*)**.
Alternatively, use continuous assignments (**assign**)
 - Synthesis tools generally fix this and issue a warning, but simulation won't work
- Use only blocking assignments
 - However, blocking assignments for internal calculations (variables used only internally in the **always** block) and non-blocking assignments for the outputs of the **always** block (signals used as inputs to other blocks) could be useful with some simulators such as Vivado
- Every **reg** must be assigned a meaningful value (not something like $Z \leq Z$;) for every possible combination of inputs (i.e., all branches of **if** / **case** statements)
- A **reg** appearing on both LHS and RHS within an **always** block should appear on the LHS before RHS. A **reg** assigned using non-blocking assignment should not appear on the RHS of the same block
 - Not really an issue if ***** is used in sensitivity list
 
```
always @ (X)
begin
if(~X)
    Z = Y;
end
```



```
always @ (*)
begin
if(X)
    Z = 1'b0;
else
    Z = Y;
end
```




[#]Inputs and outputs in this slide and the following 2 slides refer to inputs and outputs of the block we are implementing, not necessarily that of the module. Inputs are system inputs or outputs from another block. Outputs are system outputs or inputs to another block.

II : Synchronous



Synchronous : output changes only on the rising or falling edge of a single clock

- Only **posedge/negedge** CLK should be present in the sensitivity list
- Only **regs** that change on the same edge of the same clock should be assigned in the **always** block (different time => different **always** blocks)
- Use non-blocking assignments for the outputs of the **always** block (signals), as well as for any internal physical registers
 - Keep in mind that the updated values are not available for use at the same clock edge
 - Internal physical registers can also be implemented using blocking assignments where the variable appears on RHS before LHS (not recommended)
- Use blocking assignments for internal combinational parts (variables). In this case, the variable should appear on the LHS before RHS
 - However, it is not a bad idea to move combinational parts into a separate **always / assign**

 

```
always @ (posedge CLK)  
begin
```

```
//your code here  
tmp = X | Y; // tmp is a combinational variable  
Z <= tmp;    // Z is an output (signal)  
// Z <= X | Y; is fine as well
```


```
end
```

III : Synchronous with asynch set / reset



All the rules applicable for the previous template, plus

- Only **posedge/negedge** CLK and **posedge/negedge** SET/RST should be present in the sensitivity list
- Inside the **if** statement, output should be assigned a vector of **0**'s and **1**'s, and nothing more should be done
- All other code (i.e., the synchronous portion) should be inside the **else** (**begin** and **end** of **else**). There should not be additional *outer if / else ifs*
- It is fine to have additional **ifs** *inside* the synchronous part though. These **ifs** need not have **else** (why?)
- Try to **AVOID** using this - asynch. set/reset is usually avoidable, especially in FPGA designs

 

```
always @ (posedge CLK or posedge RST)
begin
if(RST)
    Z <= 1'b0;
    //do not have anything else here
else begin
    //the rest of the code goes here
    Z <= X | Y;
end
```


Physical Registers Are Inferred When ...


- Non-blocking assignments of **regs** in a synchronous **always** block
 - Their value changes on the ACT, and is not available for use until the next ACT
- Blocking assignment of **regs** in the synchronous part of an **always** block where they are read (on RHS) before being written (on LHS)*
 - They need to retain information between ACTs
 - Inferring registers this way is not recommended
 - Else, synthesized as wires or combinational circuits. Not all **regs** infer physical registers!
- *Blocking assignment also infers a register if the **reg** is an output, i.e., is on the RHS of a statement in another block. Nevertheless, DO NOT write code to infer registers this way
- If there are two registers storing identical content, they could be merged by the synthesis tool as a part of optimization (configurable)
- If a register content is not used in a parent module, it is optimized away, along with the combinational circuits exclusively feeding it

Example : Draw the Schematic

```
assign Z = X & Y;  
always @ (posedge CLK)  
begin  
    B = A;  
    C = B ^ Z;  
    D <= C;  
    E = C;  
    A = E;  
  
end
```

Note : This design does not separate combinational and sequential parts and infers registers through blocking assignments, which are not recommended practices. This example is just for illustration of concepts

State Machines in Verilog (self-reading)

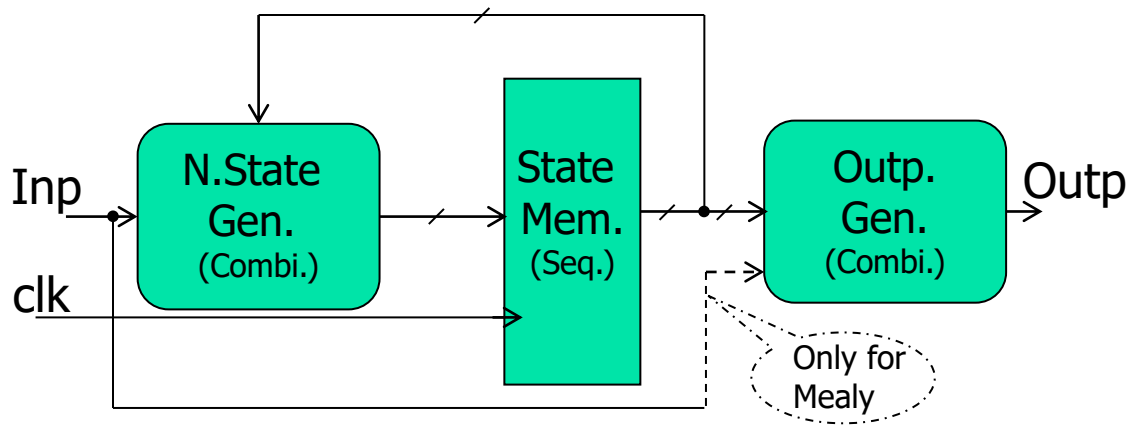

```
module SM(  
    input clk,  
    input Inp,  
    output reg Outp  
    //no reg if assigned using assign  
);  
  
    //only 1 bit required for state in the  
    //example that follows.  
    reg [0:0] state, n_state;  
    parameter S1 = 1'b0, S2 = 1'b1;  
  
    //Implementation of state memory,  
    //state and output generators  
  
endmodule
```


Note : A reset input which resets State Memory on power on is essential for ASIC designs. It is unnecessary in FPGAs as there is a dedicated Global Set/Reset (GSR) circuitry which initializes registers to their initialization values

Mealy and Moore Machines

- Mealy – output depends on input(s) and state
- Moore – output depends only on state


State	Inp	N-State	Outp
S_1	0	S_1	1
S_1	1	S_2	1
S_2	0	S_2	0
S_2	1	S_1	0

Moore

 


State	Inp	N-State	Outp
S_1	0	S_1	1
S_1	1	S_2	0
S_2	0	S_2	0
S_2	1	S_1	0

Mealy

 

Note : The 2 machines in this slide are **not** functionally equivalent

Moore Machine in Verilog

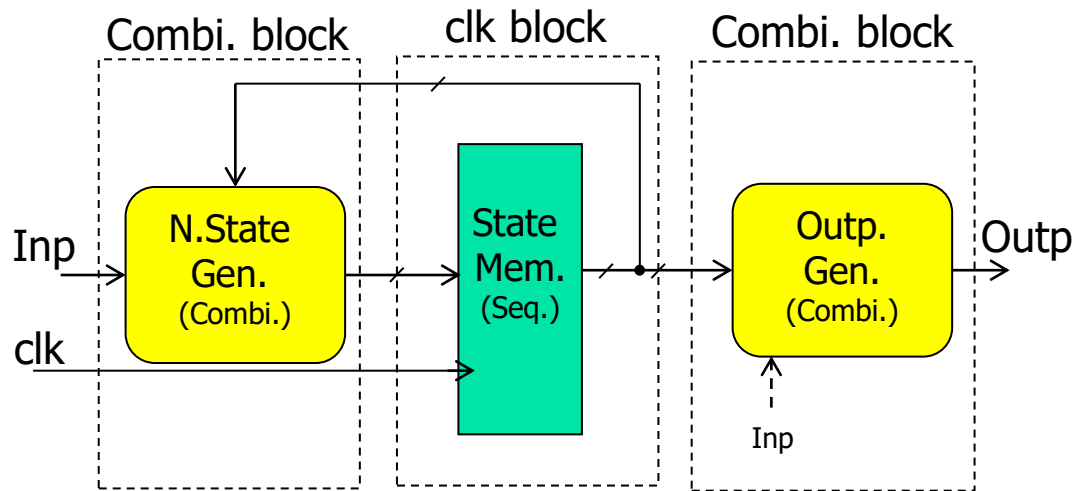

```
-- combinational block (output)
always @ (*)
begin
    case(state)
        // Outp is not a function of Inp
        S1 :
            Outp = 1'b1;
        S2 :
            Outp = 1'b0;
    endcase
end
```


```
-- clk block
always @ (posedge clk)
    state <= n_state;
```

```
-- combinational block (next state)
always @ (*)
begin
    case(state)
        S1 :
            if(Inp == 1'b0)
                begin
                    n_state = S1;
                end
            else
                begin
                    n_state = S2;
                end
        S2 :
            if(Inp == 1'b0)
                begin
                    n_state = S2;
                end
            else
                begin
                    n_state = S1;
                end
    endcase
end
```

The combinational blocks can also be implemented using [assign](#)

Moore Machine in Verilog...

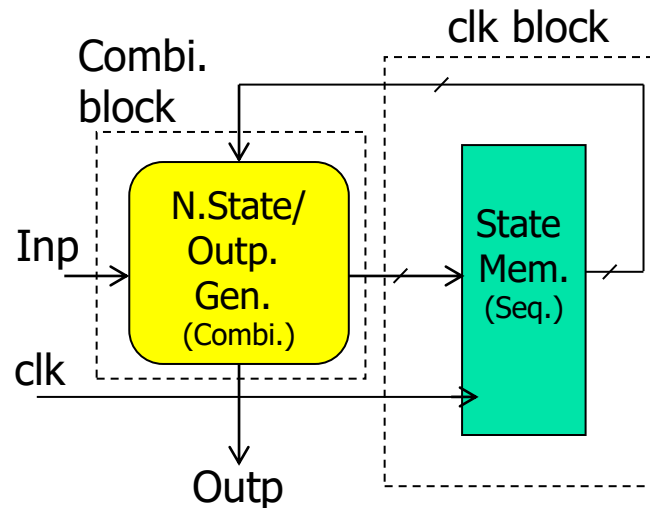- Combined next state / output generation
 - Possible savings due to combined combinational logic optimization (depends on synthesis tool settings)



```
-- clk block  
always @ (posedge clk)  
    state <= n_state;
```

```
-- combinational block  
always @ (*)  
begin  
    case(state)  
        // Outp is not a function of Inp  
    S1 :  
        Outp = 1'b1;  
        if(Inp == 1'b0)  
        begin  
            n_state = S1;  
        end  
        else  
        begin  
            n_state = S2;  
        end  
    S2 :  
        Outp = 1'b0;  
        if(Inp == 1'b0)  
        begin  
            n_state = S2;  
        end  
        else  
        begin  
            n_state = S1;  
        end  
    endcase  
end
```

Mealy Machine in Verilog

```
-- clk block
always @ (posedge clk)
    state <= n_state;
```

- Can you implement a single always block

- Mealy machine?
- Moore machine?

Hint : A clocked always block should contain only those outputs which change on a particular clock edge

```
-- combinational block
always @ (*)
begin
    case(state)
        // Outp *is* dependent on Inp
        S1 : if(Inp == 1'b0)
            begin
                n_state = S1;
                Outp = 1'b1;
            end
        else
            begin
                n_state = S2;
                Outp = 1'b0;
            end
        S2 : if(Inp == 1'b0)
            begin
                n_state = S2;
                Outp = 1'b0;
            end
        else
            begin
                n_state = S1;
                Outp = 1'b0;
            end
        endcase
    end
```